

**TRƯỜNG ĐẠI HỌC BÁCH KHOA  
ĐẠI HỌC QUỐC GIA THÀNH PHỐ HỒ CHÍ MINH  
KHOA ĐIỆN – ĐIỆN TỬ**



**LOGIC SYNTHESIS AND VLSI FRONT-END FLOW**

**Môn: THIẾT KẾ VI MẠCH**

Giảng Viên Hướng Dẫn: TRẦN HOÀNG QUÂN



# I. LOGIC SYNTHESIS

## Lab 2:

Design and synthesize “4-bit counter” specified in the previous RTL and verification lab, use verification plan in previous lab.

### 1. Code

```
module counter_4bit(clk, rst_n, sel, Q);
    input clk;
    input rst_n;
    input sel;
    output [3:0] Q;
    wire [3:0] Qn;
    wire w1, w2, w3, w4, w5, w6, w7;
    wire [3:0] J, K;
    assign J[0] = 1;
    assign K[0] = 1;
    not G1(w1, sel);
    and G2(w2, Q[0], sel);
    and G3(w3, Qn[0], w1);
    or G4(J[1], w2, w3);
    assign K[1] = J[1];

    and G5(w4, Q[1], w2);
    and G6(w5, Qn[1], w3);
    or G7(J[2], w4, w5);
    assign K[2] = J[2];

    and G8(w6, Q[2], w4);
    and G9(w7, Qn[2], w5);
    or G10(J[3], w6, w7);
    assign K[3] = J[3];

    jk_flip_flop jk_ff0 (.J(J[0]), .K(K[0]), .clk(clk), .rst_n(rst_n), .Q(Q[0]), .Qn(Qn[0]));
    jk_flip_flop jk_ff1 (.J(J[1]), .K(K[1]), .clk(clk), .rst_n(rst_n), .Q(Q[1]), .Qn(Qn[1]));
    jk_flip_flop jk_ff2 (.J(J[2]), .K(K[2]), .clk(clk), .rst_n(rst_n), .Q(Q[2]), .Qn(Qn[2]));
    jk_flip_flop jk_ff3 (.J(J[3]), .K(K[3]), .clk(clk), .rst_n(rst_n), .Q(Q[3]), .Qn(Qn[3]));
endmodule
```

## 2. Code testbench

```
module testbench;
  wire [3:0] Q;
  reg clk, rst_n, sel;
  synth_wrapper uut (
    .clk(clk),
    .rst_n(rst_n),
    .sel(sel),
    .Q(Q)
  );
  initial begin
    $shm_open("waves.shm");
    $shm_probe("AS");
  end
  initial begin
    #0 clk = 1;
    forever #5 clk = ~clk;
  end
  initial begin
    #0 rst_n = 0;      // Assert reset
    #10 rst_n = 1;     // Deassert reset after 10ns
  end

  initial begin
    #0;
    apply_stimulus(1'b1); // Enable counting
    #50;
    apply_stimulus(1'b0); // Disable counting
    #50;
    apply_stimulus(1'b1); // Enable counting again
    #50;
    apply_stimulus(1'b1); // Keep counting
    #100;
    $finish; // End simulation
  end
  task apply_stimulus(input s);
    @(posedge clk);
    sel = s;
  endtask

endmodule
```

Dưới đây là tập lệnh Makefile trong bài lab này:

```
#####  
#  
#Tuan Hung  
#HCMUT LAB3 counter_4bit  
#  
#####  
PHONY: syn  
syn: clean  
      genus -f ./03_synth/genus_shell.tcl  
#####  
#GUI = -gui  
tb_file := 01_tb/testbench.v  
  
PHONY: sim  
sim:  
      xrun $(GUI) +xm64bit -sv \
```

```

        -f 00_src/flist.f \
        $(tb_file) \
        -timescale 1ns/10ps \
        +access+rcw
#####
#GUI = -gui
delay_mode := -delay_mode punit
#sdf_file := -sdf_cmd_file 03_synth/sdf.cmd
netlist := 03_synth/*_gate.v
test_file := 01_tb/testbench.v

PHONY: verify
verify:
    xrun $(GUI) +xm64bit -sv \
    $(netlist) \
    $(test_file) \
    -vlogext .sv \
    -f 02_sim/flist.f \
    $(sdf_file) \
    $(delay_mode) \
    -timescale 1ns/10ps \
    +access+rcw

#####
PHONY: report
report:
    @echo "with Frequency at: "
    @grep "set FREQ_GHz" 03_synth/genus_shell.tcl
    @grep "Path " 04_reports/*.timing.rpt

#####
PHONY: clean
clean:
    @rm -rf genus.cmd genus.log xrun.history xrun.key xcelium.d *.shm

#####
PHONY: clean-all
clean-all: clean-rpt clean-syn
    @rm -rf fv genus.cmd genus.log xrun.history xrun.log xrun.key
counter_4bit.sdf.X xcelium.d *.shm

#####
PHONY: clean-rpt

```

clean-rpt:

```
@rm -rf 04_reports/* .rpt
```

#####

PHONY: clean-syn


clean-syn:

```
@rm -rf 03_synth/* .v 03_synth/* .sdf
```

#####


### 3. Simulation

- Result make sim:

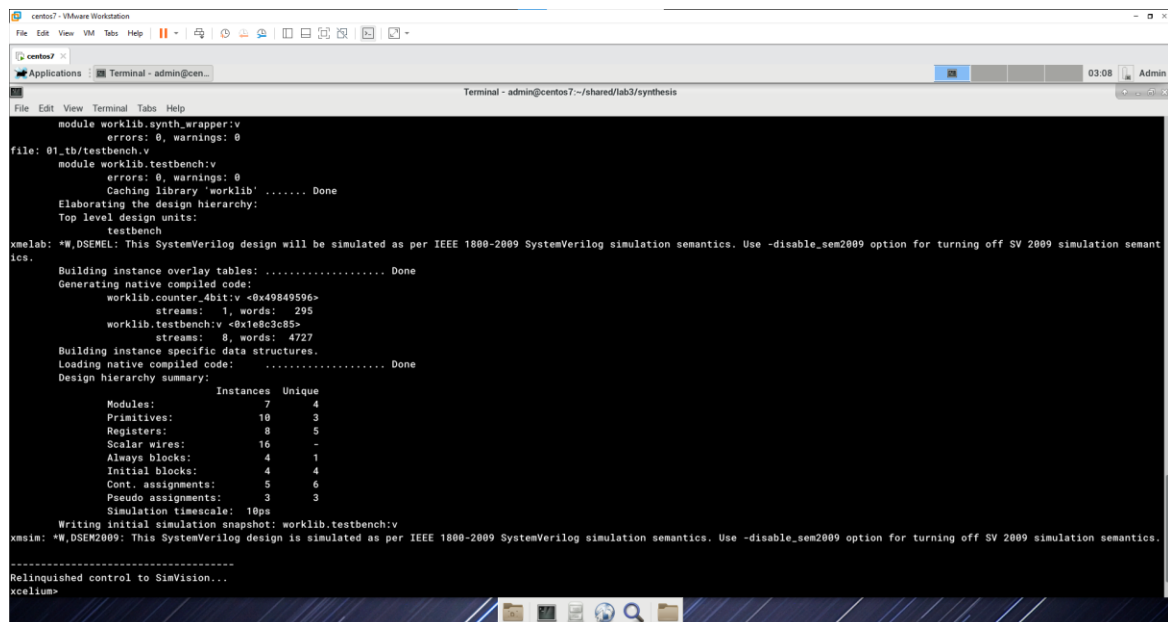

```
centos7 - VMware Workstation
File Edit View VM Tabs Help
Applications Terminal - admin@cen... 03:08 Admin
Terminal - admin@centos7:~/shared/lab3/synthesis
File Edit View Terminal Tabs Help
module worklib.synth_wrapper.v
errors: 0, warnings: 0
file: 01_tb/testbench.v
module worklib.testbench.v
errors: 0, warnings: 0
Caching library 'worklib' ..... Done
Elaborating the design hierarchy:
Top level design units:
testbench
xmelab: *W_DSEML: This SystemVerilog design will be simulated as per IEEE 1800-2009 SystemVerilog simulation semantics. Use -disable_sen2009 option for turning off SV 2009 simulation semantics.
Building instance overlay tables: ..... Done
Generating native compiled code:
worklib.counter_4bit.v <0x49849596>
streams: 1, words: 295
worklib.testbench.v <0x1e8c3c85>
streams: 8, words: 4727
Building instance specific data structures.
Loading native compiled code: ..... Done
Design hierarchy summary:
Instances Unique
Modules: 7 4
Primitives: 10 3
Registers: 8 5
Scalar wires: 16 -
Always blocks: 4 1
Initial blocks: 4 4
Cont. assignments: 5 6
Pseudo assignments: 3 3
Simulation timescale: 10ps
Writing initial simulation snapshot: worklib.testbench.v
xasim: *W_DSEM2009: This SystemVerilog design is simulated as per IEEE 1800-2009 SystemVerilog simulation semantics. Use -disable_sem2009 option for turning off SV 2009 simulation semantics.
-----
Relinquished control to SimVision...
xcellium>
```

- Kết quả mô phỏng:

 


Verification plan:

Section	Item	Descreption	Status
1	Reset	When rst_n is asserted, the output is 0, when it de-asserts, the output start to count up each positive edge of clock	PASS
2	Max count	When output is 4'b1111 and the counter is counting up, the next positive edge clock output will be 4'b0000	PASS
3	Min count	When output is 4'b0000 and the counter is counting down, the next positive edge clock output will be 4'b1111	PASS

#### 4. High level Arichitecture of the design

- Schematic của netlist:



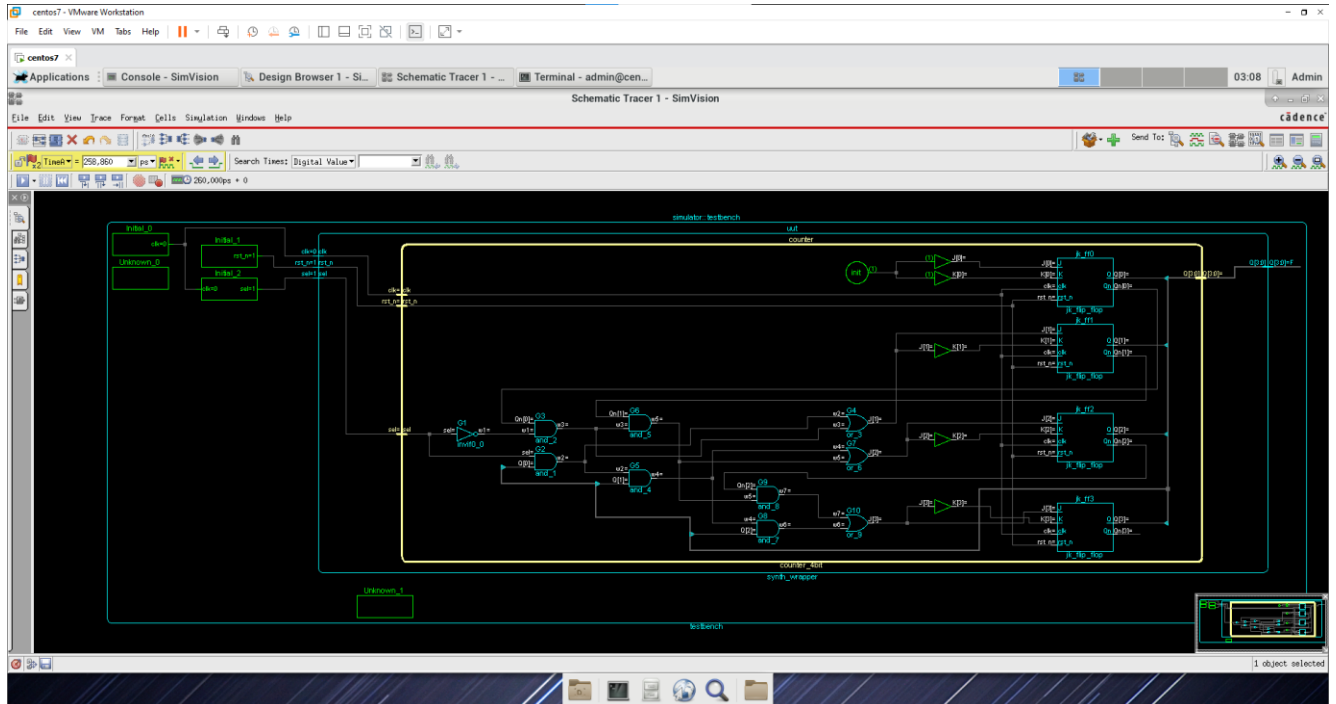

- Mô tả ngõ vào/ra:


Signal	Width	Type	Description
Clk	1	input	Clock signal

Rst_n	1	input	Negative edge reset. If rst_n = 0, output will be set to 0. Else, it will start the normal operation.
Sel	1	input	Mode selection signal. If sel = 1, the design will start counting up. Else, it will start counting down from the current output value.
Out	4	output	Result of the counter.

- Sử dụng Flip Flop JK và các cổng Not, And, Or để thực hiện đếm lên hoặc đếm xuống trong bộ counter\_4bit.

## 5. Report

- Schematic Viewer (main)

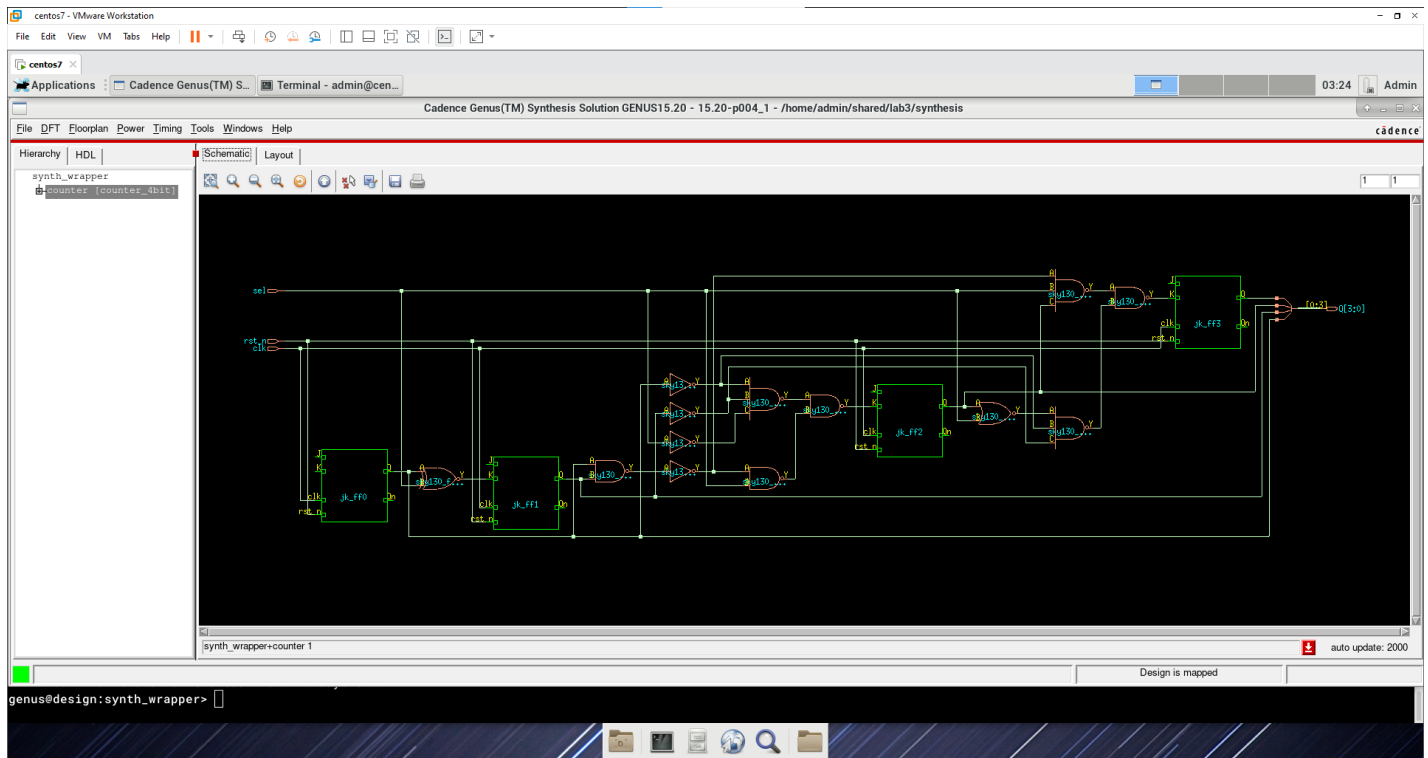

- Tần số cao nhất mà thiết kế có thể đạt được là 0.98 GHz

```
#####
#Timing constraint variables#
set FREQ_GHz 0.98
set FREQ [ expr ${FREQ_GHz} * 1000000000.0 ]
set PERIOD_tmp [ expr (1.0/${FREQ}) ]
set PERIOD [ expr ${PERIOD_tmp} * 1000000000000.0 ]
puts "Clock Period = ${PERIOD} ps"
set IN_DLY [ expr $PERIOD/2.0 ]
set OUT_DLY [ expr $PERIOD/2.0 ]
set UNCER [expr ${PERIOD}/100000.0]
puts "Clock Uncertainty = ${UNCER} ns"
set TRANS 1.5
puts "max transition = ${TRANS} ns"
#####
```

- Báo cáo tiên độ thiết kế:

```
[admin@centos7 synthesis]$ make report
with Frequency at:
set FREQ_GHz 1.1
Path 1: VIOLATED (-1 ps) Setup Check with Pin counter/jk_ff3/Q_reg/CLK->D
Path 2: MET (5 ps) Setup Check with Pin counter/jk_ff2/Q_reg/CLK->D
Path 3: MET (36 ps) Late External Delay Assertion at pin Q[0]
Path 4: MET (37 ps) Setup Check with Pin counter/jk_ff1/Q_reg/CLK->D
Path 5: MET (55 ps) Late External Delay Assertion at pin Q[1]
Path 6: MET (55 ps) Late External Delay Assertion at pin Q[2]
Path 7: MET (68 ps) Late External Delay Assertion at pin Q[3]
Path 8: MET (132 ps) Setup Check with Pin counter/jk_ff0/Q_reg/CLK->D
[admin@centos7 synthesis]$
```

- Báo cáo cũng có thể được tìm thấy trong 04\_report/counter\_4bit.timing.rpt

```

=====
Generated by:      Genus(TM) Synthesis Solution GENUS15.20 - 15.20-p004_1
Generated on:      May 24 2024  08:42:05 am
Module:            counter_4bit
Interconnect mode: global
Area mode:         timing library
=====

```

Path 1: MET (1 ps) Setup Check with Pin ff2/Qn\_reg/CLK->D

Startpoint: (R) ff0/Q\_reg/CLK

Clock: (R) clk

Endpoint: (F) ff2/Qn\_reg/D

Clock: (R) clk

	Capture	Launch
Clock Edge:+	1020	0
Src Latency:+	0	0
Net Latency:+	0 (I)	0 (I)
Arrival:=	1020	0
Setup:-	298	
Uncertainty:-	10	
Required Time:=	712	
Launch Clock:-	0	
Data Path:-	711	
Slack:=	1	

```

#-----
# Timing Point  Flags  Arc  Edge      Cell      Fanout Load Trans Delay Arrival
#                                     (fF)  (ps)  (ps)  (ps)
#-----
ff0/Q_reg/CLK -      -      R      (arrival)      7      -      0      -      0
ff0/Q_reg/Q   -      CLK->Q F      sky130_fd_sc_hd__dftrtp_1  5 14.6  92  394  394
g9/Y          -      A->Y R      sky130_fd_sc_hd__clkinv_2  3 13.2  41  65  460
g100/Y        -      A->Y F      sky130_fd_sc_hd__nand2_1   1  5.4  49  59  518
g22/Y         -      A2->Y R     sky130_fd_sc_hd__o21ai_2   2  8.3 141 143  661
ff2/g35/Y     -      A->Y F      sky130_fd_sc_hd__inv_2     2  5.9  38  50  711
ff2/Qn_reg/D  -      -      F      sky130_fd_sc_hd__sdfstp_1  2      -      -      0  711
#-----

```

- We can also see other aspects of the synthesized design in other reports inside the 04\_reports folder.

```

synthesis/04_reports
|-- counter_4bit.area.rpt
|-- counter_4bit.datapath.rpt
|-- counter_4bit.gates.rpt
|-- counter_4bit.hier.rpt
|-- counter_4bit.power.rpt
|-- counter_4bit.qor.rpt
`-- counter_4bit.timing.rpt

```

- Tổng diện tích thiết kế và tài nguyên cổng được sử dụng trong thiết kế:

```

counter_4bit.qor.rpt - Mousepad
File Edit Search View Document Help
Area mode:      timing library
=====

Timing
-----

Clock Period
-----
clk  1020.0

Cost      Critical      Violating
Group    Path Slack TNS    Paths
-----
default      1.1    0      0
-----
Total              0      0

Instance Count
-----
Leaf Instance Count      34
Sequential Instance Count 7
Combinational Instance Count 27
Hierarchical Instance Count 4

Area
----
Cell Area      341.578
Physical Cell Area 0.000
Total Cell Area (Cell+Physical) 341.578
Net Area      158.200
Total Area (Cell+Physical+Net) 499.778

Max Fanout      7 (clk)
Min Fanout      1 (J[3])
Average Fanout    2.1
Terms to net ratio 3.0
Terms to instance ratio 3.1
Runtime      10.993 seconds
Elapsed Runtime 12 seconds
RC peak memory usage: 439.77
EDI peak memory usage: no_value
Hostname      centos7

```

## Quality of Results report (QoR)



## II. VLSI FRONT-END FLOW

### Lab: ALU

#### 1. Code

```
module ALU(  
    input [3:0] A,  
    input [3:0] B,  
    input [2:0] ALU_Sel, // Selection input to choose operation  
    output reg [3:0] ALU_Out,  
    output reg Zero      // Zero flag if output is zero  
);  
  
always @(A or B or ALU_Sel) begin  
    case(ALU_Sel)  
        3'b000: ALU_Out = A + B;          // Add  
        3'b001: ALU_Out = A - B;          // Subtract  
        3'b010: ALU_Out = A & B;           // AND  
        3'b011: ALU_Out = A | B;           // OR  
        3'b100: ALU_Out = A ^ B;           // XOR  
        3'b101: ALU_Out = ~A;              // NOT (Only A is considered)  
        3'b110: ALU_Out = A << 1;          // Shift left (A)  
        3'b111: ALU_Out = A >> 1;          // Shift right (A)  
        default: ALU_Out = 4'b0000;  
    endcase  
    Zero = (ALU_Out == 4'b0000);          // Set Zero flag if ALU_Out is 0  
end  
endmodule
```

---

## 2. Code testbench

```
`timescale 1ns/10ps
module testbench;
    reg [3:0] A;
    reg [3:0] B;
    reg [2:0] ALU_Sel;
    wire [3:0] ALU_Out;
    wire Zero;
    synth_wrapper uut (.A(A), .B(B), .ALU_Sel(ALU_Sel), .ALU_Out(ALU_Out), .Zero(Zero));
    initial begin
        A = 4'b0011; // 3
        B = 4'b0001; // 1
        ALU_Sel = 3'b000; // Select addition
        #10; // Wait for operation
        $display("Add: A=%b, B=%b, ALU_Out=%b, Zero=%b", A, B, ALU_Out, Zero);
        A = 4'b0101; // 5
        B = 4'b0010; // 2
        ALU_Sel = 3'b001; // Select subtraction
        #10;
        $display("Sub: A=%b, B=%b, ALU_Out=%b, Zero=%b", A, B, ALU_Out, Zero);
        A = 4'b1100; // 12
        B = 4'b1010; // 10
        ALU_Sel = 3'b010; // Select AND
        #10;
        $display("AND: A=%b, B=%b, ALU_Out=%b, Zero=%b", A, B, ALU_Out, Zero);
        A = 4'b1100; // 12
        B = 4'b0010; // 2
        ALU_Sel = 3'b011; // Select OR
        #10;
        $display("OR: A=%b, B=%b, ALU_Out=%b, Zero=%b", A, B, ALU_Out, Zero);
        A = 4'b1010; // 10
        B = 4'b0101; // 5
        ALU_Sel = 3'b100; // Select XOR
        #10;
        $display("XOR: A=%b, B=%b, ALU_Out=%b, Zero=%b", A, B, ALU_Out, Zero);
        A = 4'b1111; // 15
        ALU_Sel = 3'b101; // Select NOT
        #10;
        $display("NOT: A=%b, ALU_Out=%b, Zero=%b", A, ALU_Out, Zero);
        A = 4'b0001; // 1
        ALU_Sel = 3'b110; // Select Shift Left
        #10;
        $display("Shift Left: A=%b, ALU_Out=%b, Zero=%b", A, ALU_Out, Zero);
        A = 4'b1000; // 8
        ALU_Sel = 3'b111; // Select Shift Right
        #10;
        $display("Shift Right: A=%b, ALU_Out=%b, Zero=%b", A, ALU_Out, Zero);
        $stop;
    end
endmodule
```




### 3. Verification plan

Section	Item	Decription	Status
1	Reset	Khi rst_n = 0, thì giá trị ngõ ra và cờ carry = 0, khi rst_1 = 1 thì mạch hoạt động bình thường.	PASS
2	Max add	Khi thực hiện việc cộng 2 số 4 bit, thì giá trị ngõ ra có thể bị tràn bit. Lúc bị tràn thì cờ carry sẽ lên 1.	PASS
3	Min sub	Khi thực hiện việc trừ 2 số 4 bit, thì giá trị ngõ ra có thể bị âm. Lúc giá trị âm thì cờ carry sẽ lên 1	PASS
4	And, or, xor, not	Thực hiện and, or, xor, not hai số 4 bit bất kì	PASS
5	Shift	Thực hiện shift right hoặc left hai số 4 bit bất kì	PASS

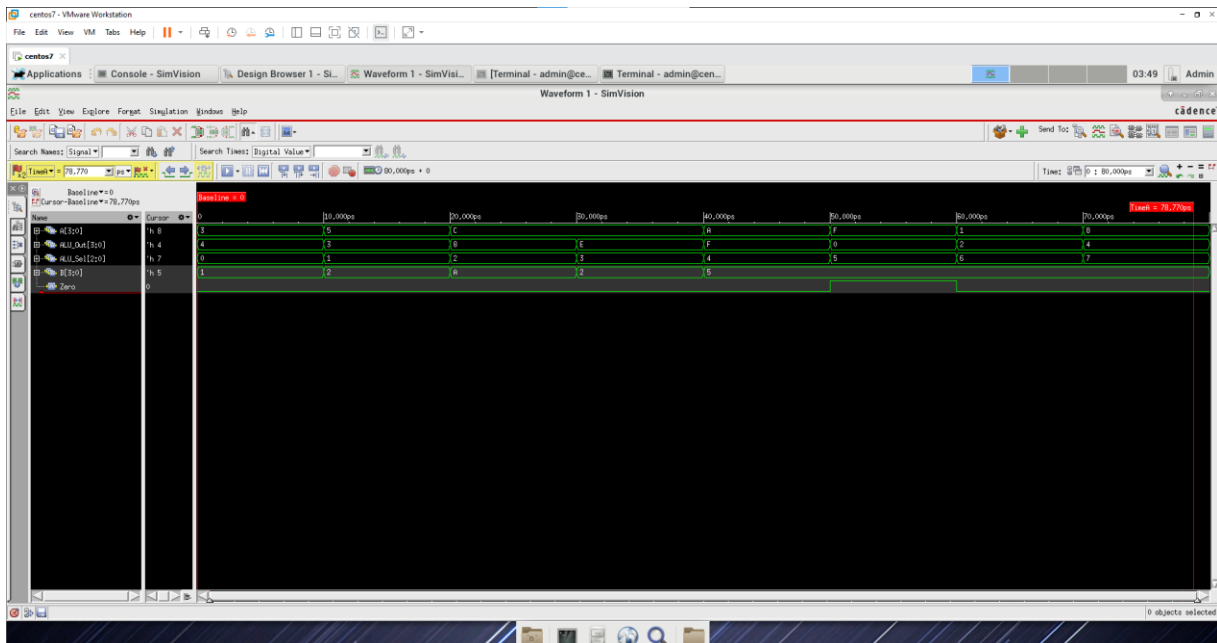
### 4. Simulation

Simulation (test add, sub, and, or, xor, not)



## 5. High level Arichitecture of the design

### - Schematic của netlist

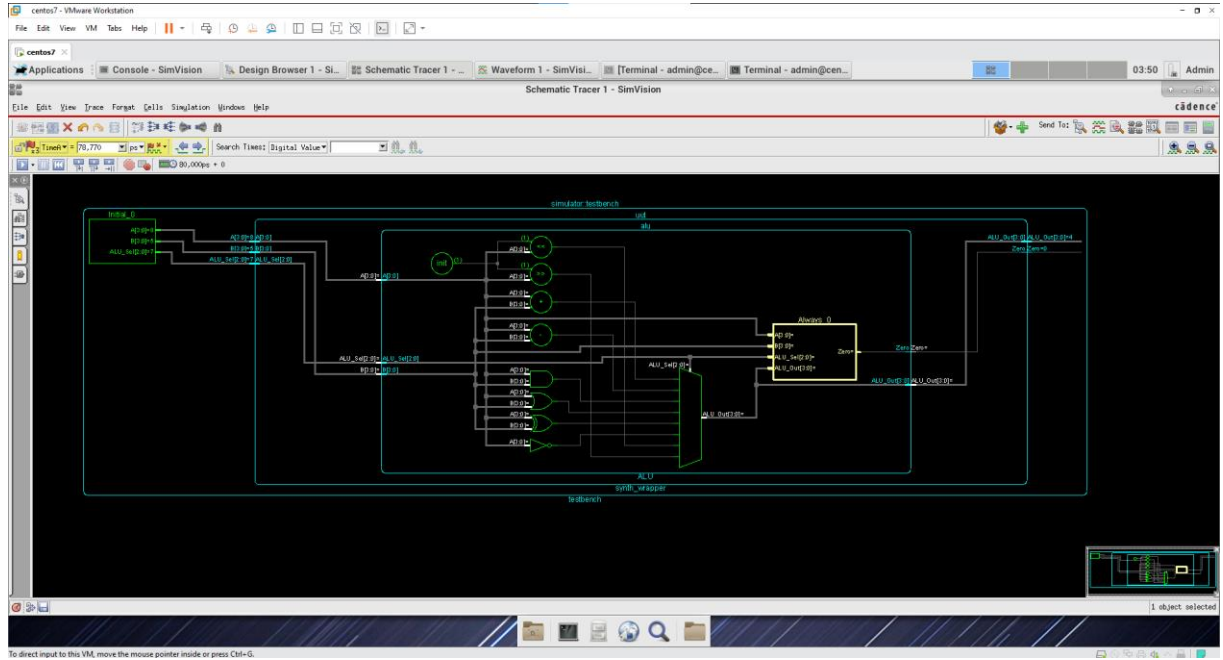

## 6. Report

- Schematic Viewer (main)

